

Lista 2 Sistemas digitais

①

a. $f(A, B, C) = A \cdot B \cdot (\bar{B} + C) + A \cdot \bar{C} + B$

Usando a Tabela verdade Tem-se que

| A B C | A.B.($\bar{B}+C$) | f |
|-------|---------------------|-------------------------------------|
| 0 0 0 | 0 | 0 |
| 0 0 1 | 0 | 0 |
| 0 1 0 | 0 | 1 — $\bar{A} \cdot B \cdot \bar{C}$ |
| 0 1 1 | 0 | 1 — $\bar{A} \cdot B \cdot C$ |
| 1 0 0 | 0 | 0 |
| 1 0 1 | 0 | 1 — $A \cdot \bar{B} \cdot C$ |
| 1 1 0 | 0 | 1 — $A \cdot B \cdot \bar{C}$ |
| 1 1 1 | 1 | 1 — $A \cdot B \cdot C$ |

$$f_{sq} = \bar{A} \cdot B \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C} + A \cdot B \cdot C$$

b. $f(A, B, C, D) = A + B + \bar{A} \cdot D + \bar{A} \cdot \bar{B}$

| A B C D | f | A B C D | f |
|---------|---|---------|---|
| 0 0 0 0 | 1 | 1 0 0 0 | 1 |
| 0 0 0 1 | 1 | 1 0 0 1 | 1 |
| 0 0 1 0 | 1 | 1 0 1 0 | 1 |
| 0 0 1 1 | 1 | 1 0 1 1 | 1 |
| 0 1 0 0 | 1 | 1 1 0 0 | 1 |
| 0 1 0 1 | 1 | 1 1 0 1 | 1 |
| 0 1 1 0 | 1 | 1 1 1 0 | 1 |
| 0 1 1 1 | 1 | 1 1 1 1 | 1 |

TAUTOLOGIA

$$c. f(A, B, C, D) = A \cdot B \cdot C + \overline{A} \cdot C \cdot B + D$$

| A B C D | f | A B C D | f |
|---------|--|---------|---|
| 0 0 0 0 | 0 | 1 0 0 0 | 0 |
| 0 0 0 1 | 1 $\overline{A} \cdot \overline{B} \cdot \overline{C} \cdot D$ | 1 0 0 1 | 1 $A \cdot \overline{B} \cdot \overline{C} \cdot D$ |
| 0 0 1 0 | 0 | 1 0 1 0 | 0 |
| 0 0 1 1 | 1 $\overline{A} \cdot \overline{B} \cdot C \cdot D$ | 1 0 1 1 | 1 $A \cdot \overline{B} \cdot C \cdot D$ |
| 0 1 0 0 | 1 $\overline{A} \cdot B \cdot \overline{C} \cdot \overline{D}$ | 1 1 0 0 | 1 $A \cdot B \cdot \overline{C} \cdot \overline{D}$ |
| 0 1 0 1 | 1 $\overline{A} \cdot B \cdot \overline{C} \cdot D$ | 1 1 0 1 | 1 $A \cdot B \cdot \overline{C} \cdot D$ |
| 0 1 1 0 | 1 $\overline{A} \cdot B \cdot C \cdot \overline{D}$ | 1 1 1 0 | 1 $A \cdot B \cdot C \cdot \overline{D}$ |
| 0 1 1 1 | 1 $\overline{A} \cdot B \cdot C \cdot D$ | 1 1 1 1 | 1 $A \cdot B \cdot C \cdot D$ |

$$f_{SP} = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot D + \overline{A} \cdot \overline{B} \cdot C \cdot D + \overline{A} \cdot B \cdot \overline{C} \cdot \overline{D} + \\ + \overline{A} \cdot B \cdot \overline{C} \cdot D + \overline{A} \cdot B \cdot C \cdot \overline{D} + \overline{A} \cdot B \cdot C \cdot D + \\ + A \cdot \overline{B} \cdot \overline{C} \cdot D + A \cdot \overline{B} \cdot C \cdot D + A \cdot B \cdot \overline{C} \cdot \overline{D} + \\ + A \cdot B \cdot \overline{C} \cdot D + A \cdot B \cdot C \cdot \overline{D} + A \cdot B \cdot C \cdot D$$


② A, B, C, D

$$\begin{cases} V(A)=1, \text{ máxima } A \text{ para de funcionar} \\ V(B)=1, \text{ máxime } B \text{ para de funcionar} \\ V(C)=1, \text{ máximas } C \text{ para de funcionar} \\ V(D)=1, \text{ máximas } D \text{ para de funcionar} \end{cases}$$

$S' = f(A, B, C, D) = 1$, linha para de
funciones

| A B C D | | A B C D | |
|---------|-------------------------------------|---------|-------------------------------|
| 0 0 0 0 | 1 $\bar{A}.\bar{B}.\bar{C}.\bar{D}$ | 1 0 0 0 | 1 $A.\bar{B}.\bar{C}.\bar{D}$ |
| 0 0 0 1 | 0 | 1 0 0 1 | 0 |
| 0 0 1 0 | 1 $\bar{A}.\bar{B}.C.\bar{D}$ | 1 0 1 0 | 0 |
| 0 0 1 1 | 0 | 1 0 1 1 | 0 |
| 0 1 0 0 | 1 $\bar{A}.B.\bar{C}.\bar{D}$ | 1 1 0 0 | 1 $A.B.\bar{C}.\bar{D}$ |
| 0 1 0 1 | 0 | 1 1 0 1 | 0 |
| 0 1 1 0 | 1 $\bar{A}.B.C.\bar{D}$ | 1 1 1 0 | 0 |
| 0 1 1 1 | 0 | 1 1 1 1 | 0 |


| | $\bar{A}\bar{B}$ | $\bar{A}B$ | AB | $A\bar{B}$ | |
|------------------|------------------|------------|------|------------|-------------------|
| $\bar{C}\bar{D}$ | 1 | 1 | 1 | 1 | $\bar{C}.\bar{D}$ |
| $\bar{C}D$ | 0 | 0 | 0 | 0 | |
| $C\bar{D}$ | 0 | 0 | 0 | 0 | |
| CD | 1 | 1 | 0 | 0 | $A.\bar{D}$ |

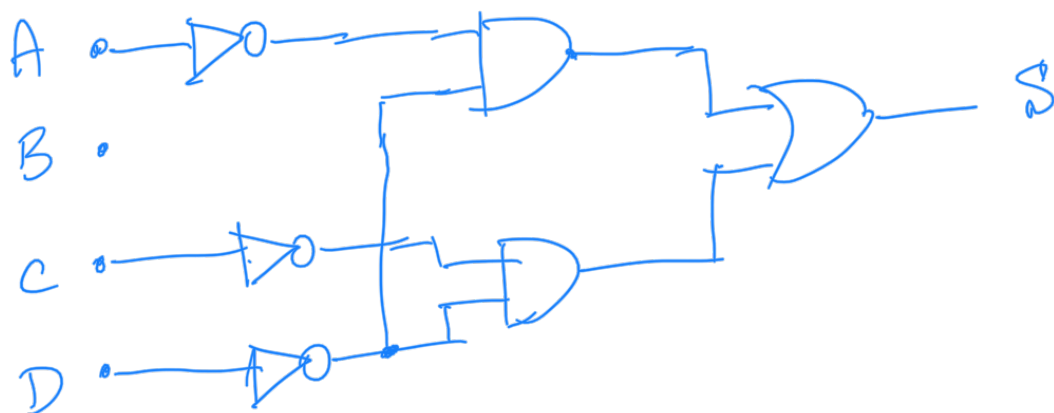

OUTRA solução q usa DS TABELA

$$S' = 0, \quad A.C + D \Rightarrow$$

$$S' = 1, \quad \underline{A.C + D}$$

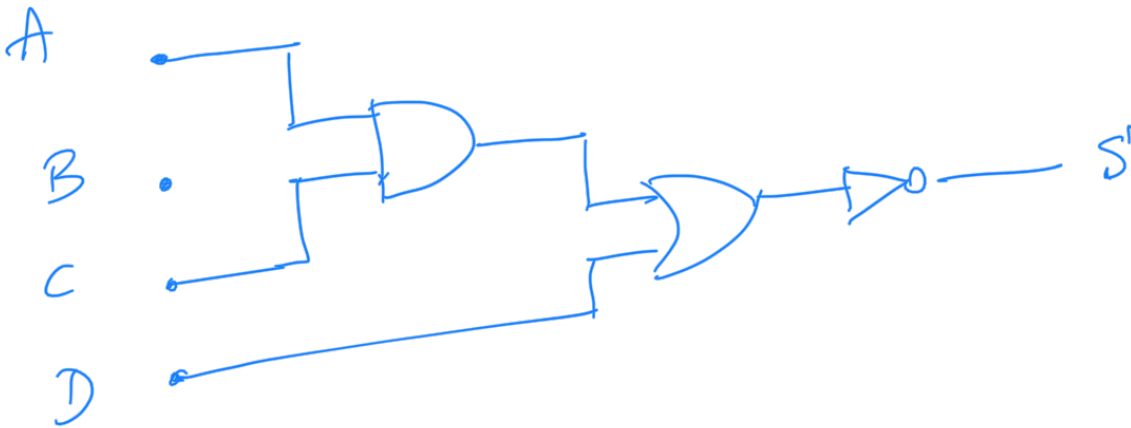

③

S_1 :: traco $3 \times R\$ 1,00$
 $1 \times R\$ 0,50$
 $1 \times R\$ 0,25$

$$S_1(A, B, C) = 1, \quad \underline{A + B}$$

S'_2 :: traco $2 \times R\$ 1,00$
 $1 \times R\$ 0,50$
 $1 \times R\$ 0,25$

$$S_2(A, B, C) = 1, \quad \underline{A.B + \underbrace{A.C + C}_{A.B + C}}$$


$S_3 \therefore$ Troco $3 \times R\$ 1,00$
 $1 \times R\$ 0,25$

$$S_3(A, B, C) = 1, \underline{B, C}$$

$S_4 \therefore$ Troco $2 \times R\$ 1,00$

$$S_4(A, B, C) = 1, \underline{A, B, C}$$


Circuito de controle

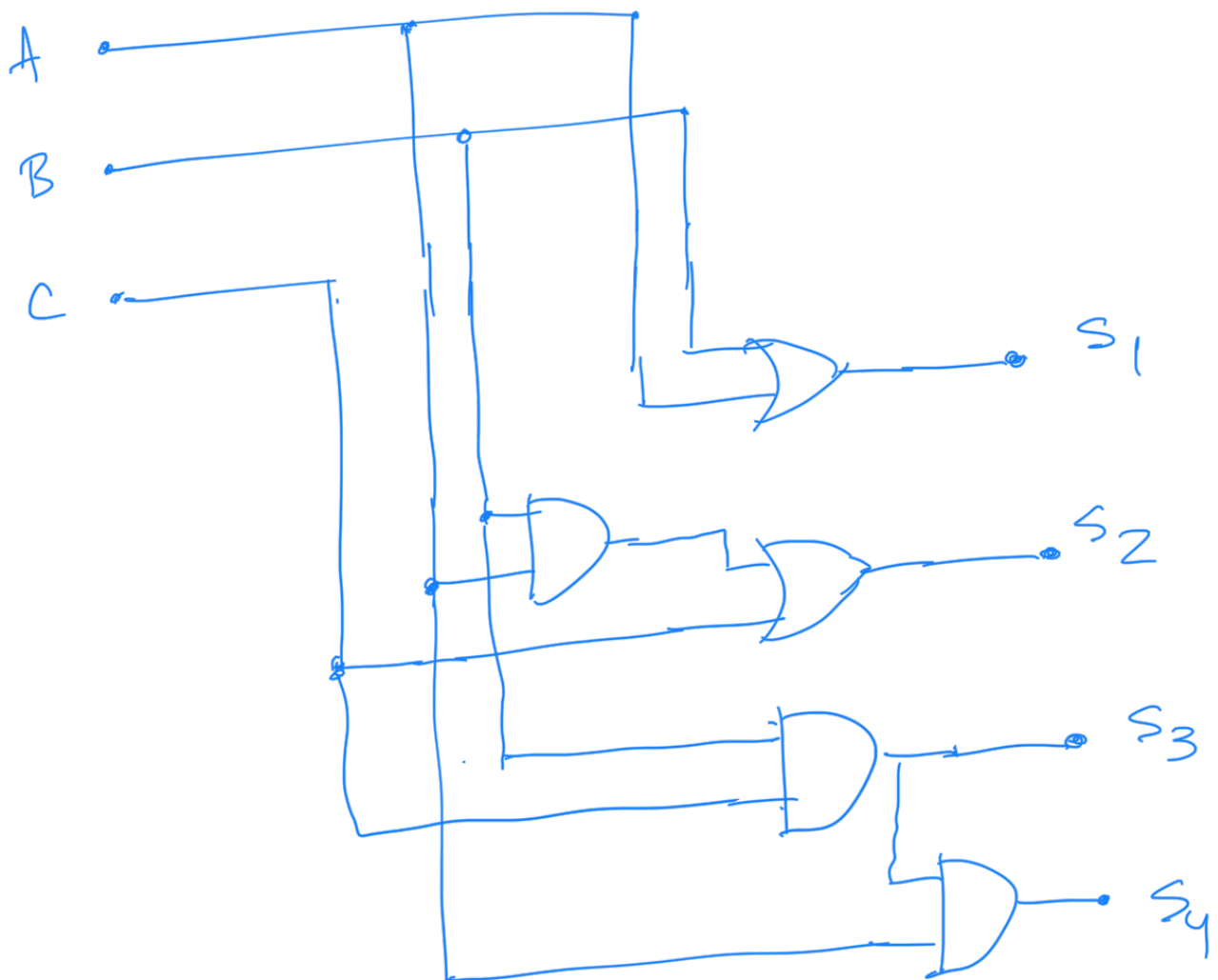

④ 1.a.

| | $\bar{A}\bar{B}$ | $\bar{A}B$ | AB | $A\bar{B}$ | |
|-----------|------------------|------------|------|------------|-------------------|
| C | 0 | 1 | 1 | 1 | $\rightarrow A.C$ |
| \bar{C} | 0 | 1 | 1 | 0 | |


B

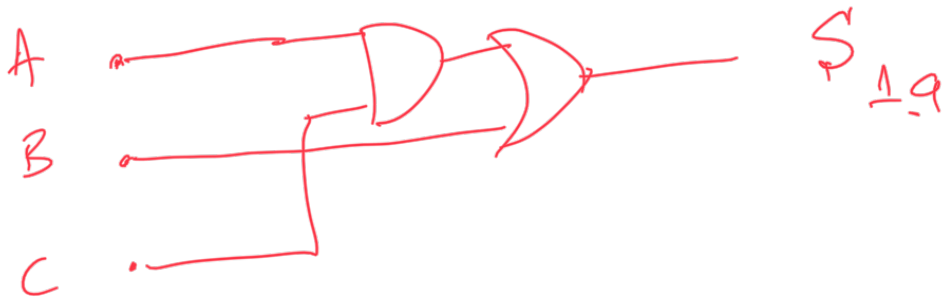

1.c

| | $\bar{A}\bar{B}$ | $\bar{A}B$ | AB | $A\bar{B}$ | |
|------------------|------------------|------------|------|------------|-----------------|
| $\bar{C}\bar{D}$ | 0 | 1 | 1 | 0 | $\rightarrow D$ |
| $\bar{C}D$ | 1 | 1 | 1 | 1 | |
| CD | 1 | 1 | 1 | 1 | |
| $C\bar{D}$ | 0 | 1 | 1 | 0 | |


B

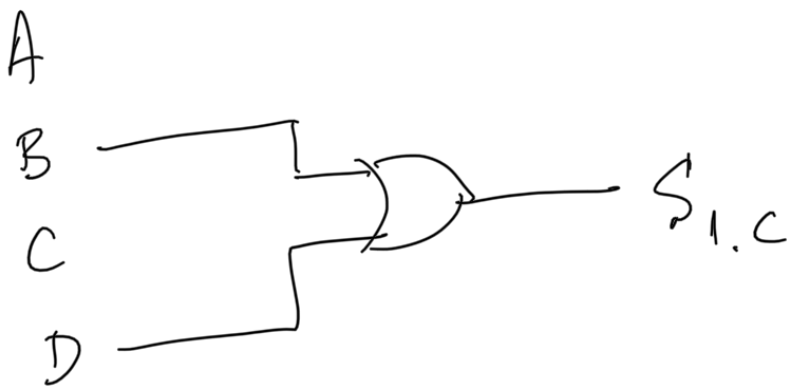


5

$$\overline{X} = \overline{X \cdot X} \rightarrow \text{circuit diagram showing } X \text{ connected to both inputs of an AND gate, followed by an inverter. An arrow points from the expression to the circuit.}$$
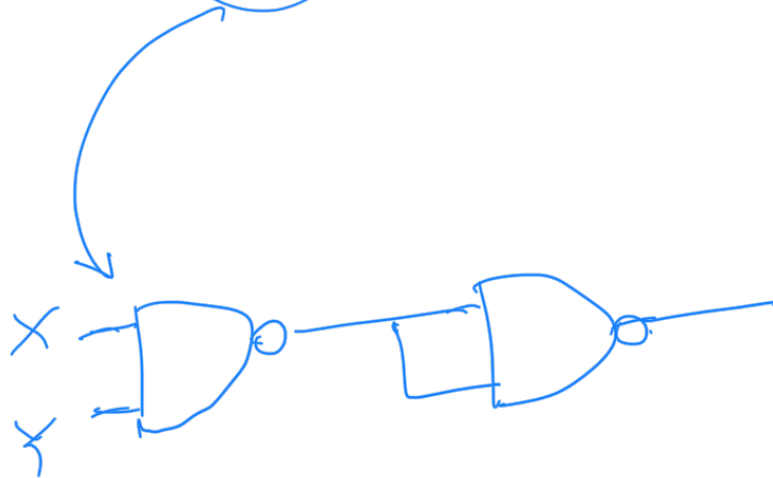
$$X \cdot Y = \overline{\overline{X \cdot Y} \cdot \overline{X \cdot Y}}$$


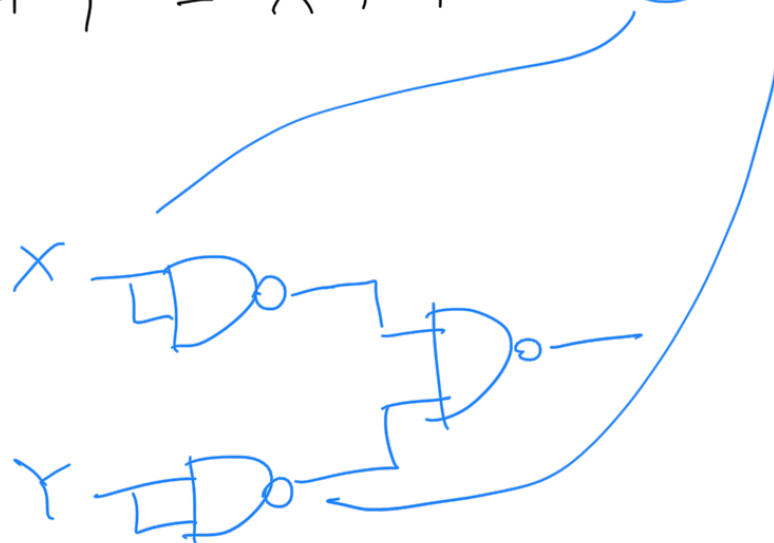
$$X + Y = \overline{\overline{X + Y}} = \overline{\overline{X} \cdot \overline{Y}}$$



fazer as substituições